

Chapter 1

DC-DC Switch-mode Converters

Dewei(David) Xu
Dept. of Electrical & Computer Engineering
Ryerson University

Content

- Introduction
- Buck converters
- One-quadrant chopper
- Two-quadrant chopper
- Review of 68HC11 MPP board
- Microprocessor control of dc-dc converters


1.1 Introduction

- Switching devices
 - The devices are operated like a switch.
 - Popular switching devices
 - SCR – silicon controlled rectifier (thyristor)
 - GTO – gate turn off thyristor
 - IGBT – insulated gate bipolar transistors
 - POWER MOSFET – metal oxide semiconductor field effect transistor

2

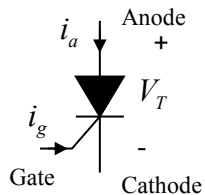1.1 Introduction

- SCR – Silicon controlled rectifier (thyristor)



i_a – Anode current

i_g – Gate current

To turn it on, $i_g > 0$

To turn it off, $V_T < 0$: (apply a reverse voltage) →
 $i_a = 0$ → the SCR is turned off.

Note: a “-ve” i_g will not turn the device off.

Device rating: $i_a = 10\text{A} \sim 6000\text{A}$

$V_T = 50\text{V} \sim 6500\text{V}$


Operating frequency: up to 500Hz

Main applications: ac-dc converters/rectifiers

3

1.1 Introduction

- GTO – Gate turn off thyristor

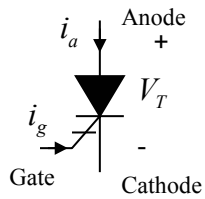

i_a – Anode current

i_g – Gate current

To turn it on, $i_g > 0$

To turn it off, $i_g < 0$

Current-controlled device

Device rating: $i_a = 10\text{A} \sim 6000\text{A}$

$V_T = 50\text{V} \sim 6000\text{V}$


Operating frequency: up to 1KHz

Main applications: high power dc-ac converters (inverters)

4

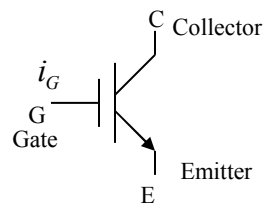1.1 Introduction

- IGBT – Insulated gate bipolar transistors



To turn it on, $V_{GE} > 0$

To turn it off, $V_{GE} < 0$

Voltage-controlled device ($i_G = 0$ at steady state)

Device rating: up to 1200A/4500V


Operating frequency: up to 20KHz

Main applications: dc-ac converters (inverters)

5

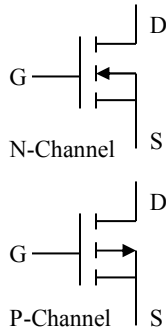1.1 Introduction

- POWER MOSFET – metal oxide semiconductor field effect transistor



- For N-Channel devices:

To turn it on, $V_{GS} > 0$

To turn it off, $V_{GS} < 0$

- For P-Channel devices:

To turn it on, $V_{GS} < 0$

To turn it off, $V_{GS} > 0$

Device rating: up to 150A/1000V

Operating frequency: up to 200KHz

Main applications: dc-dc converters (switch mode power supplies)

6

1.1 Introduction

- Device rating

| Switching devices | Single device rating (max.) | Operating frequency (max.) | Gate control |
|-------------------|-----------------------------|----------------------------|--------------|
| SCR | 4500A/6500V | 500Hz | Current |
| GTO | 4500A/6000V | 1KHz | Current |
| IGBT | 1200A/4500V | 20KHz | Voltage |
| POWER MOSFET | 150A/1000V | 200KHz | Voltage |

7


1.1 Introduction

- Summary
 - SCR and GTO are current-controlled devices. The device turn-on is controlled by gate current. SCR can NOT be turned off by applying a “-ve” gate current.
 - IGBT and POWER MOSFET are voltage-controlled devices. The device turn-on and turn-off are controlled by the gate voltage. In power converters, these devices will be either turned on (shorted) or turned off (open circuit). They NEVER operate in active mode.
 - All these devices are unidirectional.
 - In power electronics, all these devices are simplified as ideal switches:
 - when turn on, saturation voltage is zero;
 - when turn off, leakage current is zero.
 - Increase switching frequency → decrease device rating

8

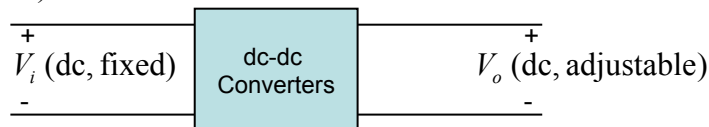1.1 Introduction

- Power converters
 - dc-dc converters (buck, boost, cuk, flyback, forward, push-pull)



V_i – dc input voltage, fixed

V_o – dc output voltage, adjustable

Main functions:


- Adjustable output voltage (dc).
- A good output voltage regulation.

- If $V_o \leq V_i \rightarrow$ Buck converter
- If $V_o \geq V_i \rightarrow$ Boost converter
- $V_o \leq V_i$ or $V_o \geq V_i \rightarrow$ Buck-boost converter, Cuk converter

9

1.1 Introduction

– ac-dc converters (rectifier)

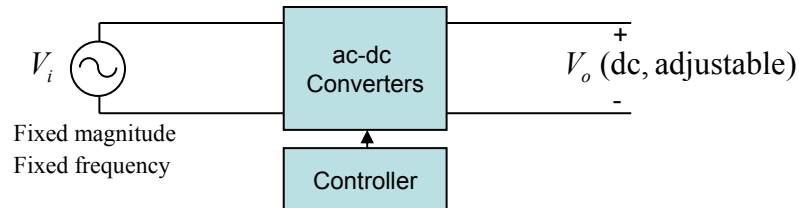

V_i – ac input voltage, fixed magnitude and fixed frequency

V_o – dc output voltage, adjustable


Main functions:

- Ac-dc conversion
- Adjustable dc output

10

1.1 Introduction

– dc-ac converters (inverters)

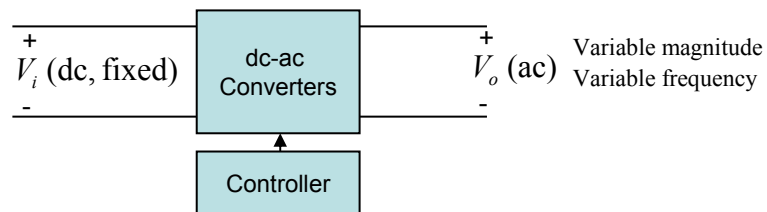

V_i – dc input voltage, fixed

V_o – ac output voltage, adjustable magnitude and adjustable frequency


Main functions:

- dc-ac conversion
- Adjustable magnitude and frequency output

11

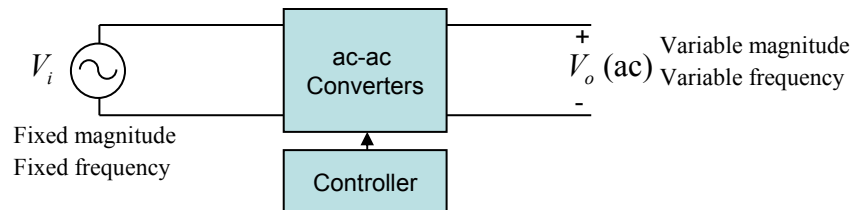1.1 Introduction

- ac-ac converters (cycloconverter, matrix converter)



V_i – ac input voltage, fixed magnitude and fixed frequency

V_o – ac output voltage, adjustable magnitude and adjustable frequency

Main functions:

- Ac-ac direct conversion
- Adjustable magnitude and frequency output

12


1.1 Introduction

- Conclusions
 - The input voltage/frequency of the converters is usually fixed
 - The output voltage/frequency of the converters is usually adjustable and regulated.
- The converters to be studied in ELE754, which are widely used in industry.
 - dc-dc converters
 - ac-dc converters
 - dc-ac converters

13

1.2 Buck Converters

- Topology

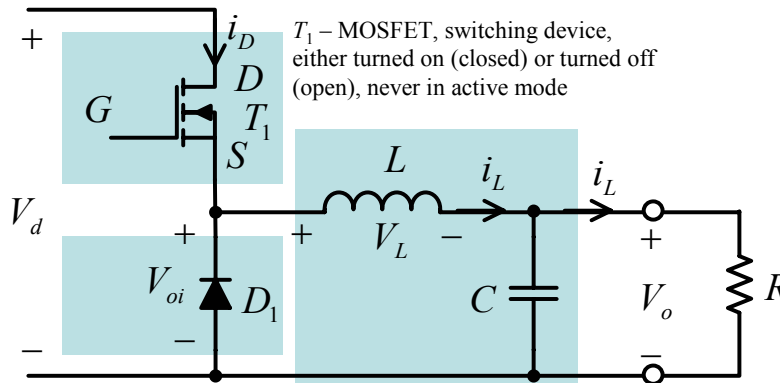

D_1 – free wheeling diode, provides current path for the current of inductor L when T_1 is off.
 L, C – Low pass filter

14

1.2 Buck Converters

- Features

- High efficiency

- Switching device loss

$$T_1 \text{ is on} \rightarrow V_{DS} \approx 0V \rightarrow P_{\text{LOSS}} = V_{DS} \times i_d \approx 0W$$

$$T_1 \text{ is off} \rightarrow i_d \approx 0A \rightarrow P_{\text{LOSS}} = V_{DS} \times i_d \approx 0W$$

- L, C and diode loss \rightarrow negligible

- Small size

- High switching frequency \rightarrow small size of L and C .

- Assumption:


- Ideal switches: $V_{DS, \text{on}} = 0V$ (MOSFET T_1) and $V_{D1, \text{on}} = 0V$ (Diode D_1)

- $C = \infty \rightarrow V_o = \text{constant}$, no voltage ripple

15

1.2 Buck Converters

- Waveforms (continuous current mode)

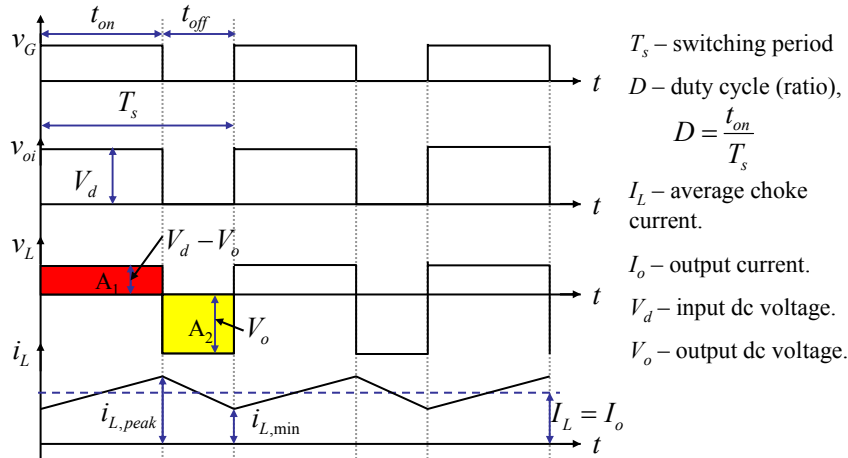

16

1.2 Buck Converters

– Summary


- T_{on} period: T_1 on $\rightarrow V_{oi} = V_d \rightarrow i_L \uparrow$, energy stored in L , $v_L = V_d - V_o$ due to $C = \infty$ and $V_o = \text{constant}$.
- T_{off} period: T_1 off \rightarrow energy in L released through C , R and $D_1 \rightarrow D_1$ is on, $v_{oi} = 0$.
- Average output current $I_o = ?$
No dc current increase $\rightarrow I_o = I_L$
- Output voltage $V_o = ?$
Ideal inductor \rightarrow No dc voltage drop on the inductor \rightarrow
Area $A_1 = \text{Area } A_2$.
 $\rightarrow (V_d - V_o)t_{on} = V_o t_{off} = V_o(T_s - t_{on})$
 $\rightarrow V_o = V_d D$
- $0 \leq D \leq 1 \rightarrow V_o \leq V_d \rightarrow$ buck converter, or step-down converter

17

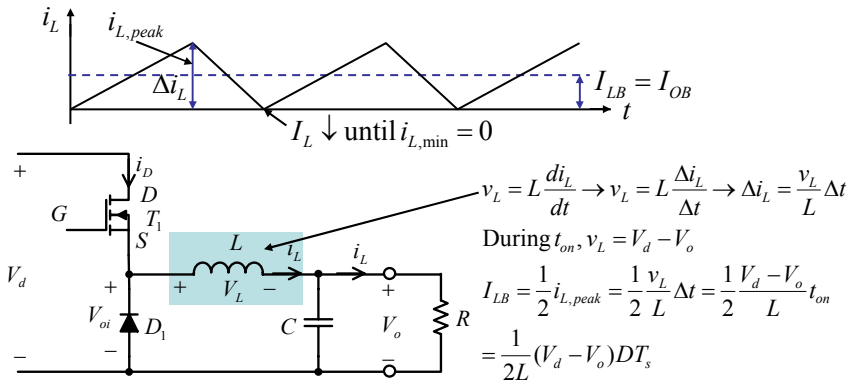1.2 Buck Converters

- Boundary between continuous and discontinuous current mode

i_L continuous → continuous current mode
 i_L discontinuous → discontinuous current mode



18

1.2 Buck Converters

- Identify the operation mode of buck converter


$$I_{LB} = \frac{1}{2L} (V_d - V_o) D T_s$$

If $I_L > I_{LB} \rightarrow$ continuous current mode

If $I_L < I_{LB} \rightarrow$ discontinuous current mode

$$\because V_o = D V_d$$

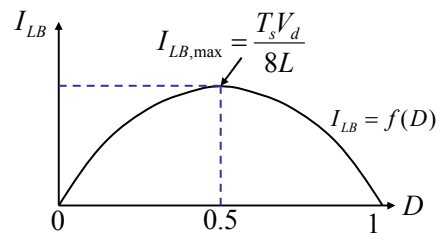
$$\therefore I_{LB} = \frac{T_s V_d}{2L} D(1-D) = f(D)$$



19

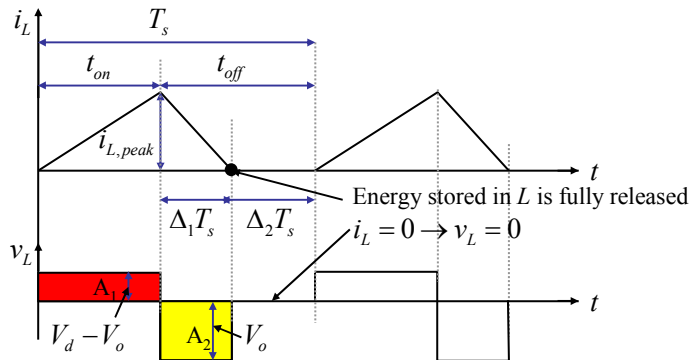1.2 Buck Converters

- Discontinuous current mode
 - Waveforms



20

1.2 Buck Converters

- Output voltage $V_o = ?$

$$\text{Area } A_1 = \text{Area } A_2$$

$$\rightarrow (V_d - V_o)DT_s = V_o\Delta_1T_s$$

$$\rightarrow V_o = \frac{D}{D + \Delta_1}V_d \quad (1)$$

$$\Delta i_L = \frac{V_L}{L}\Delta t \rightarrow i_{L,peak} = \frac{V_o}{L}\Delta_1T_s$$

$$\rightarrow \Delta_1 = \frac{Li_{L,peak}}{V_oT_s} = \frac{I_o}{4I_{LB,max}}D \quad (2)$$

$$(2) \rightarrow (1)$$

$$V_o = \frac{D^2}{D^2 + \frac{1}{4}(I_o/I_{LB,max})}V_d \quad \text{for discontinuous current mode}$$

21

1.2 Buck Converters

- Summary

- Assumption
 - Ideal switches, switching device and diode
 - Constant output voltage
- Key equations

$$\Delta i_L = \frac{V}{L} \Delta t$$

$$V_o = DV_d \text{ for continuous current mode}$$

$$V_o = \frac{D^2}{D^2 + \frac{1}{4}(I_o/I_{LB,max})} V_d \text{ for discontinuous current mode}$$

$$I_{LB} = \frac{TV_d}{2L} D(1-D) \quad I_L > I_{LB} \rightarrow \text{continuous current mode}$$

$$I_L < I_{LB} \rightarrow \text{discontinuous current mode}$$

$$I_{LB,max} = \frac{TV_d}{8L}$$

- Waveforms


- v_G, v_L, i_L

22

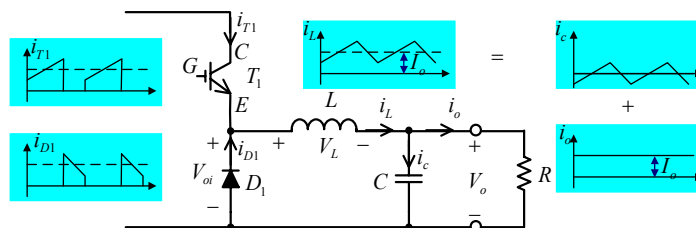1.2 Buck Converters

- Output voltage ripple


- Filter capacitance is not infinite, practical value
- Ripple voltage $\Delta V_o/V_o$ usually is less than 1%
- Assume
 - All the ripple component of inductor current flows through the capacitor.
 - The dc component of inductor current flows through the load resistor
- Pick continuous current mode as example: current waveforms



23

1.2 Buck Converters

– Voltage waveforms

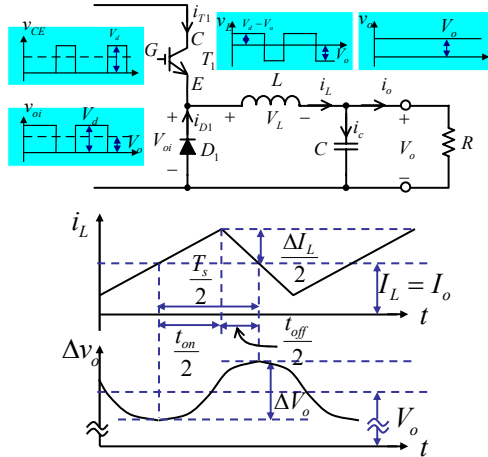

$$\Delta V_o = \frac{1}{C} \int_0^{T_s} i_c dt = \frac{1}{C} \int_0^{T_s} (i_L - I_L) dt$$

$$= \frac{1}{C} \left(\frac{\Delta I_L}{2} \frac{t_{on}}{2} \frac{1}{2} + \frac{\Delta I_L}{2} \frac{t_{off}}{2} \frac{1}{2} \right) = \frac{\Delta I_L T_s}{8C} \quad (1)$$

$$\Delta I_L = \frac{V_o}{L} (1-D) T_s \quad (2)$$

(2) → (1)

$$\Delta V_o = \frac{T_s}{8C} \frac{V_o}{L} (1-D) T_s$$

$$\frac{\Delta V_o}{V_o} = \frac{\pi^2}{2} (1-D) \left(\frac{f_c}{f_s} \right)^2 \quad (3)$$

where, $f_c = \frac{1}{2\pi\sqrt{LC}}$ is corner frequency

of LC filter and $f_s = \frac{1}{T_s}$ is switching

frequency.

24

1.2 Buck Converters

– Reduce voltage ripple


- Decrease the corner frequency → $L \uparrow$ or $C \uparrow$ → Larger size of the converter.
- Increase the switching frequency → switching loss \uparrow → efficiency \downarrow .
- How to reduce switching loss?
 - Use low switching loss device, such as MOSFET
 - Use soft switching topology, such as ZVS, ZCS)

– $f_s \approx (10 \sim 100) f_c \rightarrow \Delta V_o / V_o$ usually is less than 1%

25

Example I

• Example I

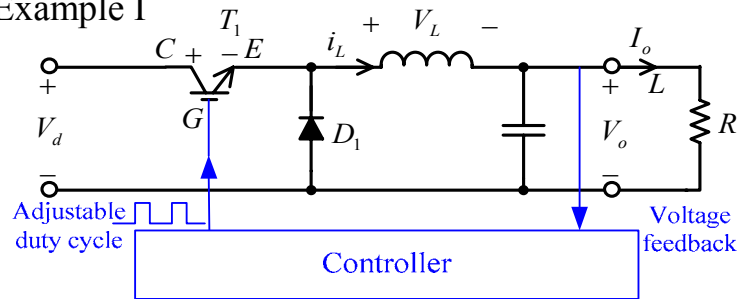

Given : $V_d = 150\text{V}$, $f_{sw} = 20\text{KHz}$, $L = 1\text{mH}$, $C = 47.0\mu\text{F}$,
 $V_o = 48\text{V}$ and load resistance $R = 10\Omega$, Assume the output voltage is kept constant.

Find : (1) operating mode, (2) ripple voltage $\frac{\Delta V_o}{V_o}$

(3) inductor's current ripple ΔI_L , (4) duty cycle if $R = 100\Omega$

26

Example I

Solution(1) :

$$\text{step 1} \Rightarrow I_o = \frac{V_o}{R} = \frac{48}{10} = 4.8\text{A}$$

$$\text{step 2} \Rightarrow I_L = I_o = 4.8\text{A}$$

$$\text{step 3} \Rightarrow \text{Assume continuous current mode: } D = \frac{V_o}{V_d} = \frac{48}{150} = 0.32$$

$$\text{step 4} \Rightarrow I_{LB} = \frac{T_s V_d}{2L} D(1-D) = \frac{50 \times 10^{-6} \times 150}{2 \times 1 \times 10^{-3}} \times 0.32 \times (1-0.32) = 0.816\text{A}$$

$$\text{where } T_s = \frac{1}{f_{sw}} = \frac{1}{20 \times 10^3} = 50 \times 10^{-6}\text{s}$$

$$\text{step 5} \Rightarrow I_L > I_{LB} \rightarrow \text{Continuous current mode}$$

27

Example I

Solution (2) :

In continuous current mode :

$$\frac{\Delta V_o}{V_o} = \frac{\pi^2}{2} (1-D) \left(\frac{f_c}{f_s} \right)^2 = \frac{\pi^2}{2} (1-0.32) \left(\frac{734.13}{20 \times 10^3} \right)^2 = 4.5 \text{mV}$$

$$\text{where } f_c = \frac{1}{2\pi\sqrt{LC}} = \frac{1}{2\pi\sqrt{1 \times 10^{-3} \times 47 \times 10^{-6}}} = 734.13 \text{Hz}$$

Solution (3) :

Current ripple

$$\Delta I_L = \frac{V_d - V_o}{L} t_{on} = \frac{V_d - V_o}{L} D T_s = \frac{150 - 48}{1 \times 10^{-3}} \times 0.32 \times 50 \times 10^{-6} = 1.632 \text{A}$$

or

$$\Delta I_L = \frac{V_o}{L} t_{off} = \frac{V_o}{L} (1-D) T_s = \frac{48}{1 \times 10^{-3}} \times (1-0.32) \times 50 \times 10^{-6} = 1.632 \text{A}$$

28

Example I

Solution (4) :

$$\text{step 1} \Rightarrow I_o = \frac{V_o}{R} = \frac{48}{100} = 0.48 \text{A}$$

$$\text{step 2} \Rightarrow I_L = I_o = 0.48 \text{A}$$

$$\text{step 3} \Rightarrow \text{Assume continuous current mode : } D = \frac{V_o}{V_d} = 0.32$$

$$\text{step 4} \Rightarrow I_{LB} = 0.816 \text{A}$$

$$\text{step 5} \Rightarrow I_L < I_{LB} \rightarrow \text{discontinuous current mode}$$

$$\text{step 6} \Rightarrow \text{use } V_o = \frac{D^2}{D^2 + \frac{1}{4} \left(\frac{I_o}{I_{LB, \max}} \right)} V_d \rightarrow$$

$$D = \sqrt{\frac{\frac{V_o}{4} \left(\frac{I_o}{I_{LB, \max}} \right)}{V_d - V_o}} = \sqrt{\frac{\frac{48}{4} (0.48/0.9375)}{150 - 48}} = 0.2454$$




$$\text{where } I_{LB, \max} = \frac{T_s V_d}{8L} = \frac{50 \times 10^{-6} \times 150}{8 \times 1 \times 10^{-3}} = 0.9375$$

29

1.3 One Quadrant Chopper

- One quadrant chopper with RL load


– Circuit diagram

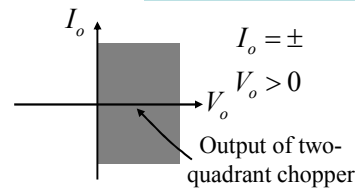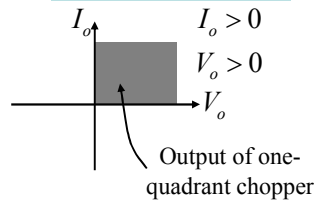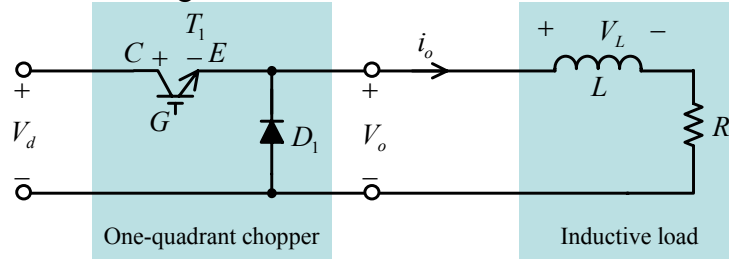

30

1.3 One Quadrant Chopper

– Waveforms

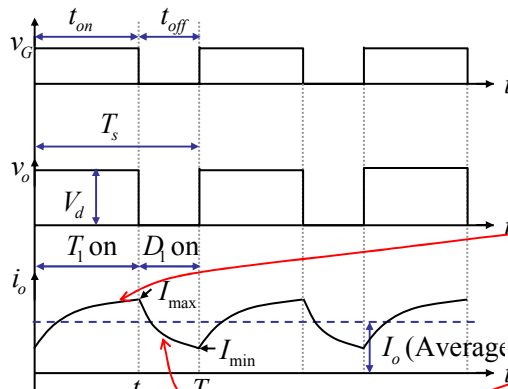

i_o does not increase or decrease linearly! when T_1 is on :

$$v_o = V_d = L \frac{di_o}{dt} + Ri_o \rightarrow$$

$$i_o(t) = \frac{V_d}{R} \left(1 - e^{-\frac{t}{\tau}} \right) + I_{min} e^{-\frac{t}{\tau}}$$

when T_1 is off (D_1 is on) :

$$v_o = 0 = L \frac{di_o}{dt} + Ri_o \rightarrow$$

$$i_o(t) = I_{max} e^{-\frac{(t-t_{on})}{\tau}}$$

where $\tau = L/R$ is time constant of inductive load

Note: $\tau \frac{dx}{dt} = -x + b \rightarrow x(t) = x_0 e^{-t/\tau} + b(1 - e^{-t/\tau})$,

where $x_0 = x(0)$ is initial value and $b = x(\infty)$ is final value.

31


1.3 One Quadrant Chopper

– I_{\max} and I_{\min}

From current waveform

$$i_o(t) = \frac{V_d}{R} \left(1 - e^{-\frac{t}{\tau}} \right) + I_{\min} e^{-\frac{t}{\tau}}, 0 \leq t < t_{on} \quad (1)$$
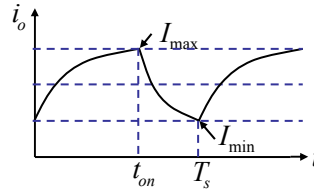
$$i_o(t) = I_{\max} e^{-\frac{(t-t_{on})}{\tau}}, t_{on} \leq t < T_s \quad (2)$$



From Eq.(1) At $t = t_{on}$, $i_o(t_{on}) = I_{\max} \rightarrow I_{\max} = \frac{V_d}{R} \left(1 - e^{-\frac{t_{on}}{\tau}} \right) + I_{\min} e^{-\frac{t_{on}}{\tau}} \quad (3)$

From Eq.(2) At $t = T_s$, $i_o(T_s) = I_{\min} \rightarrow I_{\min} = I_{\max} e^{-\frac{T_s - t_{on}}{\tau}} \quad (4)$


Solve Eq.(3) and Eq.(4)

$$I_{\max} = \frac{V_d}{R} \frac{1 - e^{-\frac{t_{on}}{\tau}}}{1 - e^{-\frac{T_s}{\tau}}} \quad \text{and} \quad I_{\min} = \frac{V_d}{R} \frac{e^{-\frac{t_{on}}{\tau}} - 1}{e^{-\frac{T_s}{\tau}} - 1}$$

32

Example II

- Example II

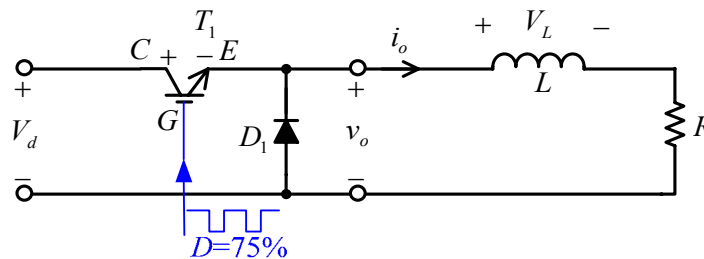

Given : one quadrant chopper with RL load (inductive load)

$V_d = 120\text{V}$, $f_{sw} = 1\text{KHz}$, $L = 4.5\text{mH}$, $R = 1.5\Omega$, $D = 0.75$

Find : (1) inductor's current ripple ΔI_L , (2) average I_o and V_o

33

Example II

Solution (1):

$$\text{step 1} \Rightarrow \tau = \frac{L}{R} = \frac{4.5 \times 10^{-3}}{1.5} = 3\text{ms}$$

$$\text{step 2} \Rightarrow T_s = \frac{1}{f_{sw}} = \frac{1}{1000} = 1\text{ms}$$

$$\text{step 3} \Rightarrow t_{on} = DT_s = 0.75 \times 1 = 0.75\text{ms}$$

$$\text{step 4} \Rightarrow I_{\max} = \frac{V_d}{R} \frac{1 - e^{-t_{on}/\tau}}{1 - e^{-T_s/\tau}} = \frac{120}{1.5} \frac{1 - e^{-0.75/3}}{1 - e^{-1/3}} = 62.4\text{A}$$

$$I_{\min} = \frac{V_d}{R} \frac{e^{t_{on}/\tau} - 1}{e^{T_s/\tau} - 1} = \frac{120}{1.5} \frac{e^{0.75/3} - 1}{e^{1/3} - 1} = 57.5\text{A}$$

$$\text{step 5} \Rightarrow \Delta I_L = I_{\max} - I_{\min} = 62.4 - 57.5 = 4.9\text{A}$$

34

Example II

Solution (2):

$$V_{o,avg} = DV_d = 0.75 \times 120 = 90\text{V}$$

$$I_{o,avg} = \frac{V_{o,avg}}{R} = \frac{90}{1.5} = 60\text{A}, \text{ (because of no dc voltage drop on the inductor)}$$


Also

$$I_{o,avg} \approx \frac{I_{\max} + I_{\min}}{2} = \frac{62.4 + 57.5}{2} = 60\text{A}$$

35

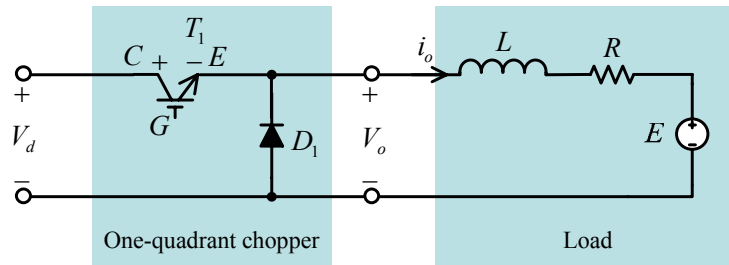1.3 One Quadrant Chopper

- One quadrant chopper with RLE load
 - Circuit diagram




Load: DC motor equivalent circuit
L: armature winding inductance
R: armature winding resistance
E: back emf

36

1.3 One Quadrant Chopper

– Waveforms (continuous current mode)

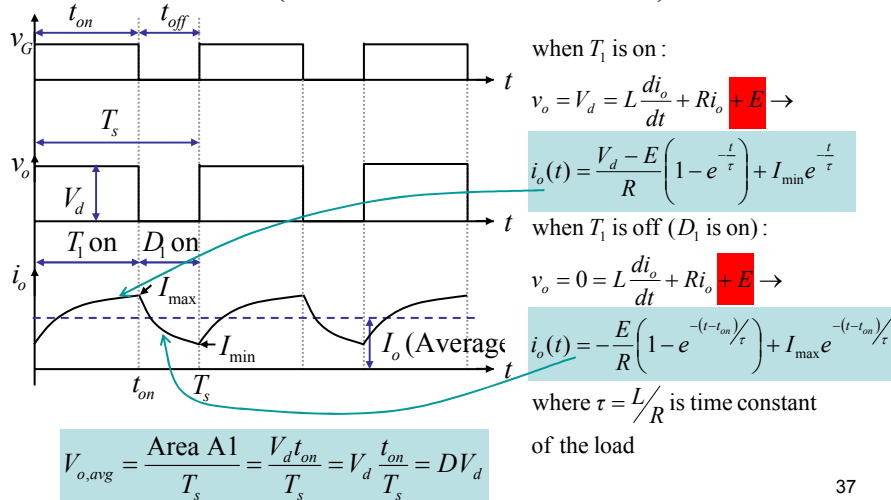

37


1.3 One Quadrant Chopper

– I_{\max} and I_{\min}

From current waveform

$$i_o(t) = \frac{V_d - E}{R} \left(1 - e^{-\frac{t}{\tau}} \right) + I_{\min} e^{-\frac{t}{\tau}}, 0 \leq t < t_{on} \quad (1)$$
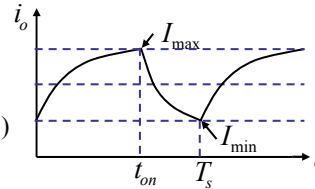
$$i_o(t) = -\frac{E}{R} \left(1 - e^{-\frac{(t-t_{on})}{\tau}} \right) + I_{\max} e^{-\frac{(t-t_{on})}{\tau}}, t_{on} \leq t < T_s \quad (2)$$



From Eq.(1) At $t = t_{on}$, $i_o(t_{on}) = I_{\max} \rightarrow I_{\max} = \frac{V_d - E}{R} \left(1 - e^{-\frac{t_{on}}{\tau}} \right) + I_{\min} e^{-\frac{t_{on}}{\tau}} \quad (3)$

From Eq.(2) At $t = T_s$, $i_o(T_s) = I_{\min} \rightarrow I_{\min} = -\frac{E}{R} \left(1 - e^{-\frac{(T_s - t_{on})}{\tau}} \right) + I_{\max} e^{-\frac{(T_s - t_{on})}{\tau}} \quad (4)$

Solve Eq.(3) and Eq.(4)


$$I_{\max} = \frac{V_d}{R} \frac{1 - e^{-\frac{t_{on}}{\tau}}}{1 - e^{-\frac{T_s}{\tau}}} - \frac{E}{R} \quad \text{and} \quad I_{\min} = \frac{V_d}{R} \frac{e^{\frac{t_{on}}{\tau}} - 1}{e^{\frac{T_s}{\tau}} - 1} - \frac{E}{R}$$

Note: continuous current mode!

38

1.3 One Quadrant Chopper

– Waveforms (discontinuous current mode)

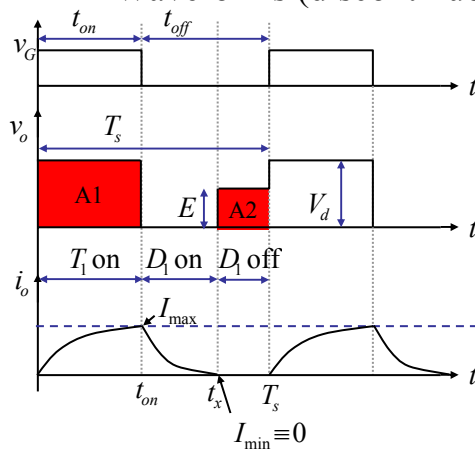

(1) $t_{on} \leq t < t_x$,

L is releasing the energy to the load
 $\rightarrow D_1$ is on $\rightarrow V_o = 0$

(2) at t_x ,

The energy in L is fully released
 $\rightarrow i_o = 0$

(3) $t_x \leq t < T_s$,

$i_o = 0 \rightarrow D_1$ is off $\rightarrow V_o = E$

$$V_{o,avg} = \frac{\text{AreaA1} + \text{AreaA2}}{T_s} = \frac{V_d t_{on} + E(T_s - t_x)}{T_s} = V_d \frac{t_{on}}{T_s} + E \frac{T_s - t_x}{T_s}$$


39

1.3 One Quadrant Chopper

– $I_{\max} = ?$ and $I_{\min} \equiv 0$

From current waveform
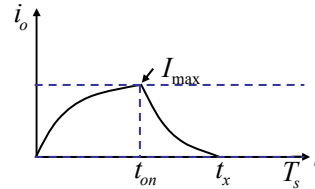
$$i_o(t) = \frac{V_d - E}{R} \left(1 - e^{-\frac{t}{\tau}} \right), 0 \leq t < t_{on} \quad (1)$$



$$i_o(t) = -\frac{E}{R} \left(1 - e^{-(t-t_{on})/\tau} \right) + I_{\max} e^{-(t-t_{on})/\tau}, t_{on} \leq t < t_x \quad (2)$$

From Eq.(1) At $t = t_{on}$, $i_o(t_{on}) = I_{\max} \rightarrow I_{\max} = \frac{V_d - E}{R} \left(1 - e^{-\frac{t_{on}}{\tau}} \right)$ (3)

From Eq.(2) At $t = t_x$, $i_o(t_x) = 0 \rightarrow 0 = -\frac{E}{R} \left(1 - e^{-(t_x-t_{on})/\tau} \right) + I_{\max} e^{-(t_x-t_{on})/\tau}$ (4)

Solve Eq.(4)

$$t_x = \tau \ln \left\{ e^{\frac{t_{on}}{\tau}} \left[1 + \frac{V_d - E}{E} \left(1 - e^{-\frac{t_{on}}{\tau}} \right) \right] \right\} \quad \text{Note: discontinuous current mode!}$$

40

1.3 One Quadrant Chopper

– Summary

• Equations

Continuous current mode :

$$V_{o,avg} = \frac{t_{on}}{T_s} V_d = DV_d$$

$$I_{o,avg} = \frac{V_{o,avg} - E}{R}$$

$$I_{\max} = \frac{V_d}{R} \frac{1 - e^{-\frac{t_{on}}{\tau}}}{1 - e^{-\frac{T_s}{\tau}}} - \frac{E}{R}$$

$$I_{\min} = \frac{V_d}{R} \frac{e^{\frac{t_{on}}{\tau}} - 1}{e^{\frac{T_s}{\tau}} - 1} - \frac{E}{R} > 0$$

• waveforms

Discontinuous current mode :

$$V_{o,avg} = \frac{t_{on}}{T_s} V_d + \frac{T_s - t_x}{T_s} E \neq DV_d$$

$$I_{o,avg} = \frac{V_{o,avg} - E}{R}$$

$$I_{\max} = \frac{V_d - E}{R} \left(1 - e^{-\frac{t_{on}}{\tau}} \right)$$


$$I_{\min} \equiv 0$$

$$t_x = \tau \ln \left\{ e^{\frac{t_{on}}{\tau}} \left[1 + \frac{V_d - E}{E} \left(1 - e^{-\frac{t_{on}}{\tau}} \right) \right] \right\}$$

41

Example III

- Example III

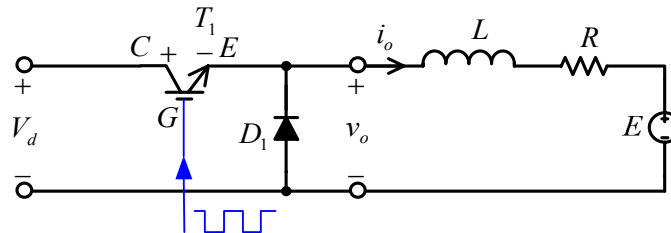

Given : one quadrant chopper drives a dc motor

$V_d = 110\text{V}$, $f_{sw} = 400\text{Hz}$, $L = 0.2\text{mH}$, $R = 0.25\Omega$, $D = 0.5$ and $E = 40\text{V}$

Find : (1) operation mode (continuous or discontinuous),

(2) I_{\max} and I_{\min} , (3) average I_o and V_o

42

Example III

Solution (1) :

step 1 \Rightarrow Assume continuous current mode

$$\text{step 2} \Rightarrow \tau = \frac{L}{R} = \frac{0.2 \times 10^{-3}}{0.25} = 0.8\text{ms}$$

$$\text{step 3} \Rightarrow T_s = \frac{1}{f_{sw}} = \frac{1}{400} = 2.5\text{ms}$$

$$\text{step 4} \Rightarrow t_{on} = DT_s = 0.5 \times 2.5 = 1.25\text{ms}$$

$$\text{step 5} \Rightarrow I_{\min} = \frac{V_d}{R} \frac{e^{t_{on}/\tau} - 1}{e^{T_s/\tau} - 1} - \frac{E}{R} = \frac{110}{0.25} \frac{e^{1.25/0.8} - 1}{e^{2.5/0.8} - 1} - \frac{40}{0.25} = -84\text{A}$$

step 6 $\Rightarrow I_{\min} < 0 \rightarrow$ discontinuous current mode

43

Example III

Solution (2) :

$$I_{\max} = \frac{V_d - E}{R} \left(1 - e^{-\frac{t_{on}}{\tau}} \right) = \frac{110 - 40}{0.25} \left(1 - e^{-1.25/0.8} \right) = 221.2 \text{ A}$$

$$I_{\min} = 0 \text{ A}$$

Solution (3) :

$$\begin{aligned} \text{step1} \Rightarrow t_x &= \tau \ln \left\{ e^{\frac{t_{on}}{\tau}} \left[1 + \frac{V_d - E}{E} \left(1 - e^{-\frac{t_{on}}{\tau}} \right) \right] \right\} \\ &= 0.8 \times 10^{-3} \left\{ e^{1.25/0.8} \left[1 + \frac{110 - 40}{40} \left(1 - e^{-1.25/0.8} \right) \right] \right\} = 1.94 \text{ ms} \end{aligned}$$


$$\text{step2} \Rightarrow V_{o,avg} = \frac{t_{on}}{T_s} V_d + \frac{T_s - t_x}{T_s} E = \frac{1.25}{2.5} \times 110 + \frac{2.5 - 1.94}{2.5} \times 40 = 64 \text{ V}$$

$$\text{step3} \Rightarrow I_{o,avg} = \frac{V_{o,avg} - E}{R} = \frac{64 - 40}{0.25} = 96 \text{ A}$$

44


1.4 Project 1 dc-dc converter

• Power Converter Module

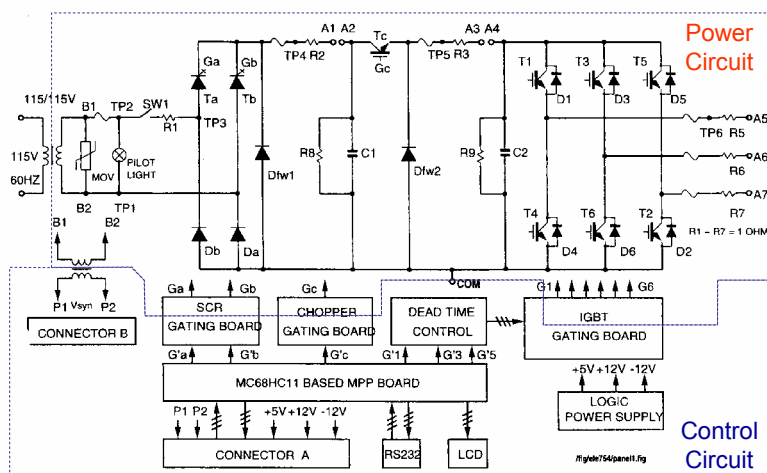

45

1.4 Project 1 dc-dc converter

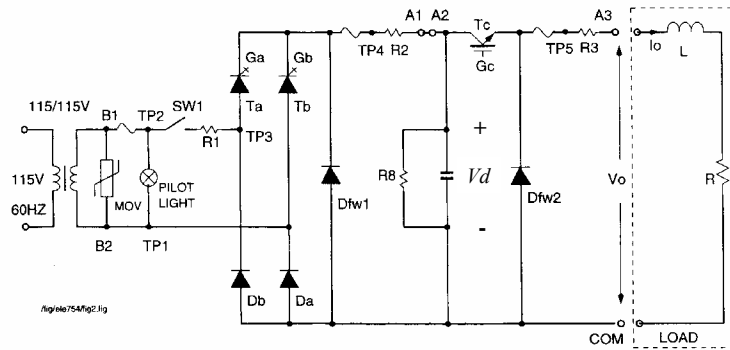

V_d – dc voltage, from SCR rectifier, A1(A2) respect to COM


R8 – discharge resistor for safety

Tc – IGBT switching device

R2, R3 – current sensing resistor, 1Ω

46

1.4 Project 1 dc-dc converter

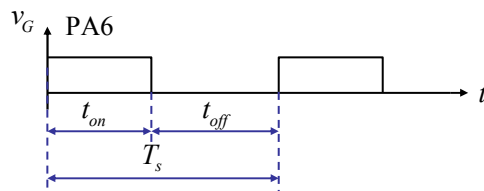

• Duty cycle control

– f_s is fixed $\rightarrow T_s$ is fixed

– D is variable $\rightarrow t_{on}$ is variable

$$[\text{TIME_HI}] = \frac{t_{on}}{T_{E-cycle}} = t_{on} \times f_{E-cycle} = DT_s f_{E-cycle}$$

$$\text{if } T_s = \frac{1}{f_{sw}} = \frac{1}{500} = 2000 \mu s, f_{E-cycle} = 1 \text{MHz}$$

$$[\text{TIME_HI}] = D \times 2000 = (100 \times D) \times 20$$

$$[\text{TIME_LO}] = (1 - D) \times 2000 = [100 - (100 \times D)] \times 20$$

47


1.4 Project 1 dc-dc converter

- Programming
 - Main program
 - All non real-time subroutines
 - Use subroutines (easy to debug, easy to read)
 - ISR (interrupt service routine)
 - Real-time running
 - As short as possible
 - Optimize the code to save CPU time

48


1.4 Project 1 dc-dc converter

- Main program flow chat

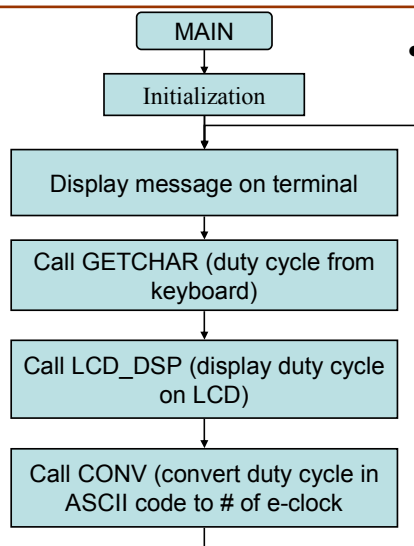

49

1.4 Project 1 dc-dc converter

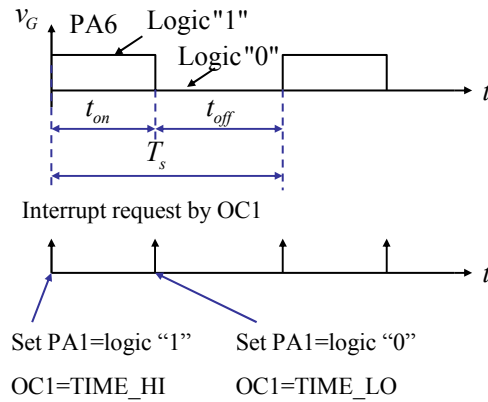


• ISR

- Set the output port PA6 to logic "0" or "1"
- Set output compare register OC1 (timer) for next interrupt
- Return to main program

50

1.4 Project 1 dc-dc converter

• Ramp function flow chart

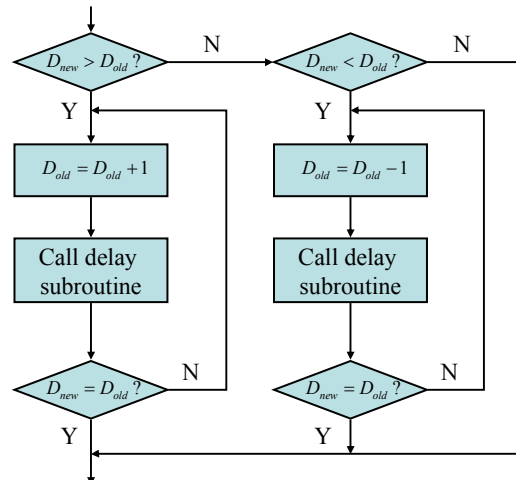


51

1.4 Project 1 dc-dc converter

- Gate signal generator

- Analog circuit
- Digital circuit

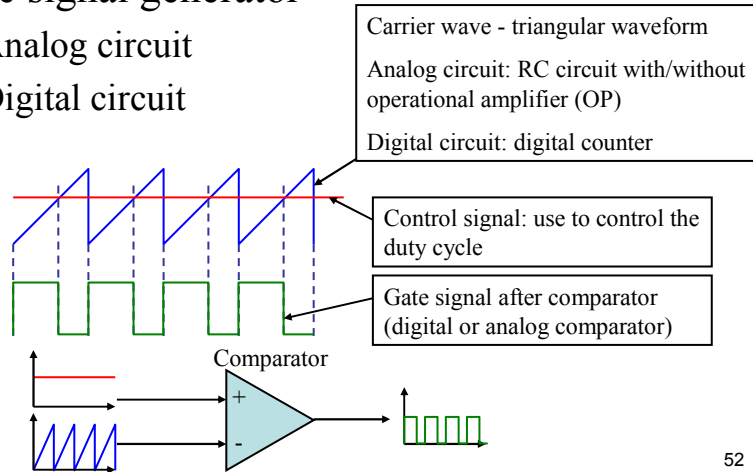

1.5 Fourier Analysis of 1Q Chopper

- Theorem

- Fourier series

$$f(t) = f_0 + \sum_{n=1}^{\infty} a_n \cos(n\omega t) + \sum_{n=1}^{\infty} b_n \sin(n\omega t)$$

$$\text{where } f_0 = \frac{1}{2\pi} \int_0^{2\pi} f(t) d(\omega t) = \frac{1}{T} \int_0^T f(t) dt \quad \leftarrow \text{dc component}$$

$$\left. \begin{aligned} a_n &= \frac{1}{\pi} \int_0^{2\pi} f(t) \cos(n\omega t) d(\omega t) = \frac{2}{T} \int_0^T f(t) \cos(n\omega t) dt \\ b_n &= \frac{1}{\pi} \int_0^{2\pi} f(t) \sin(n\omega t) d(\omega t) = \frac{2}{T} \int_0^T f(t) \sin(n\omega t) dt \end{aligned} \right\} \text{nth order harmonics}$$

also :

$$f(t) = f_0 + \sum_{n=1}^{\infty} c_n \sin(n\omega t + \theta_n) \text{ where } c_n = \sqrt{a_n^2 + b_n^2} \text{ and } \theta_n = \tan^{-1} \left(\frac{a_n}{b_n} \right) \quad 53$$


1.5 Fourier Analysis of 1Q Chopper

– Example

$$v_o = \begin{cases} V_m & 2k\pi \leq t < (2k+1)\pi \\ -V_m & (2k+1)\pi \leq t < (2k+2)\pi \end{cases}, k = 0, 1, 2, \dots$$


Fourier series :
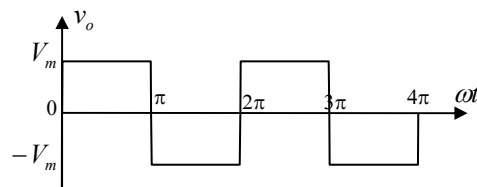
$$v_o = \sum_{n=1,3,5,\dots}^{\infty} \frac{4V_m}{n\pi} \sin(n\omega t) = \frac{4V_m}{\pi} \left(\sin \omega t + \frac{1}{3} \sin 3\omega t + \frac{1}{5} \sin 5\omega t + \dots \right)$$



54

1.5 Fourier Analysis of 1Q Chopper

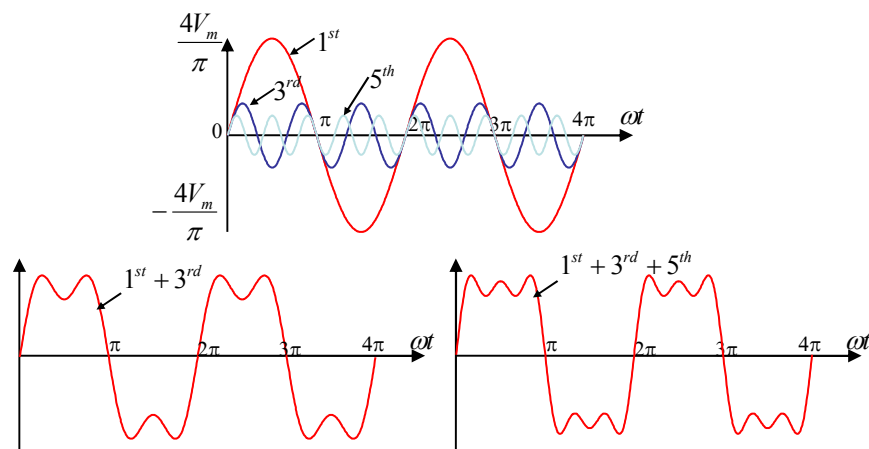


55

1.5 Fourier Analysis of 1Q Chopper

- Fourier Analysis of 1Q Chopper

- Methodology

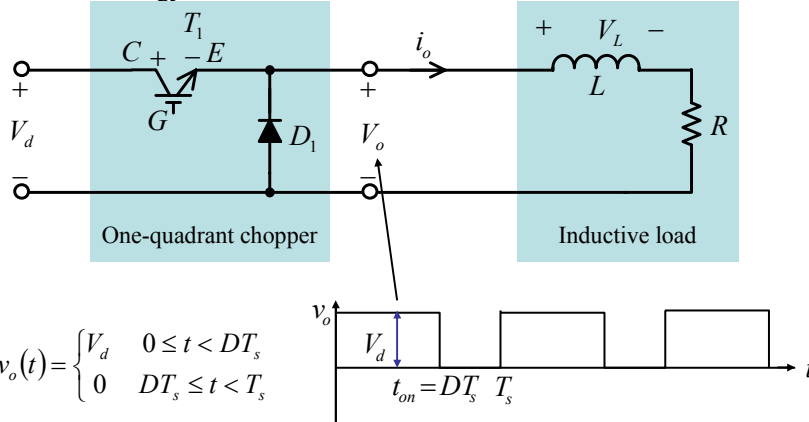

56

1.5 Fourier Analysis of 1Q Chopper

Fourier analysis :

$$V_{o,dc} = \frac{1}{T_s} \int_0^{T_s} v_o(t) dt = \frac{1}{T_s} \left(\int_0^{DT_s} V_d dt + \int_{DT_s}^{T_s} 0 dt \right) = \frac{V_d}{T_s} t \Big|_0^{DT_s} = DV_d$$

$$a_n = \frac{2}{T_s} \int_0^{T_s} v_o(t) \cos(n\omega t) dt = \frac{2}{T_s} \frac{1}{n\omega} \int_0^{DT_s} V_d \cos(n\omega t) d(n\omega t)$$

$$= \frac{2V_d}{n\omega T_s} \sin(n\omega t) \Big|_0^{DT_s} = \frac{2V_d}{n\omega T_s} \sin(n\omega DT_s) = \frac{V_d}{n\pi} \sin(2\pi nD)$$

where $\omega = 2\pi f = \frac{2\pi}{T_s}$

$$b_n = \frac{2}{T_s} \int_0^{T_s} v_o(t) \sin(n\omega t) dt = \frac{2}{T_s} \frac{1}{n\omega} \int_0^{DT_s} V_d \sin(n\omega t) d(n\omega t)$$

$$= \frac{2V_d}{n\omega T_s} [-\cos(n\omega t)] \Big|_0^{DT_s} = \frac{2V_d}{n\omega T_s} [1 - \cos(n\omega DT_s)] = \frac{V_d}{n\pi} [1 - \cos(2\pi nD)]$$

$$\therefore v_o(t) = DV_d + \frac{V_d}{n\pi} \sum_{n=1,2,3,\dots} \sin(2\pi nD) \cos(n\omega t) + \frac{V_d}{n\pi} \sum_{n=1,2,3,\dots} [1 - \cos(2\pi nD)] \sin(n\omega t)$$


57

1.5 Fourier Analysis of 1Q Chopper


– High frequency equivalent circuit



dc equivalent circuit

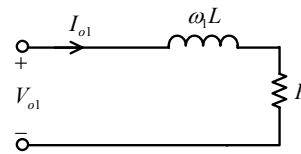

fundamental equivalent circuit

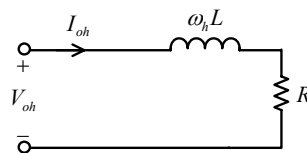

h^{th} order harmonic equivalent circuit

$$\text{where } \omega_1 = 2\pi f = \frac{2\pi}{T_s}$$


$$\omega_1 = 2\pi h f = \frac{2\pi}{T_s} h$$

58

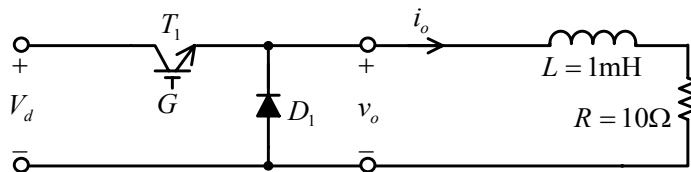Example IV

Given: 1Q chopper with RL load. $V_d=100\text{V}$, $D=0.4$, $R=10\Omega$ and $L=1\text{mH}$, the switching frequency is 1KHz.

- Find: (1) The harmonic components of v_o , up to 5th order harmonic
 (2) The harmonic components of i_o , up to 5th order harmonic



Use following formulas :

$$V_{o,dc} = DV_d, a_n = \frac{V_d}{n\pi} \sin(2\pi n D), b_n = \frac{V_d}{n\pi} [1 - \cos(2\pi n D)]$$

59

Example IV

Solution (1):

$$a_1 = \frac{V_d}{\pi} \sin(2\pi D) = \frac{100}{\pi} \sin(2\pi \times 0.4) = 18.71,$$

$$b_1 = \frac{V_d}{n\pi} [1 - \cos(2\pi D)] = \frac{100}{\pi} [1 - \cos(2\pi \times 0.4)] = 57.58$$

$$V_{o1} = \sqrt{a_1^2 + b_1^2} = \sqrt{18.71^2 + 57.58^2} = 60.55\text{V (peak)}$$

$$a_2 = \frac{V_d}{2\pi} \sin(2\pi \times 2D) = -15.15, b_2 = \frac{V_d}{2\pi} [1 - \cos(2\pi \times 2D)] = 11.00$$

$$V_{o2} = \sqrt{a_2^2 + b_2^2} = 18.71\text{V (peak)}$$

$$a_3 = 10.09, b_3 = 7.33, V_{o3} = 12.47\text{V (peak)}$$

$$a_4 = -4.68, b_4 = 14.40, V_{o4} = 15.14\text{V (peak)}$$

$$a_5 = 0, b_5 = 0, V_{o5} = 0\text{V}$$

60

Example IV

Solution (2):

$$V_{o1} = 60.55, Z_1 = \sqrt{(2\pi fL)^2 + R^2} = \sqrt{(2\pi \times 10^3 \times 1 \times 10^{-3})^2 + 10^2} = 11.81$$

$$I_{o1} = \frac{V_{o1}}{Z_1} = \frac{60.55}{11.81} = 5.13\text{A (peak)}$$

$$V_{o2} = 18.71, Z_2 = \sqrt{(2\pi \times 2fL)^2 + R^2} = \sqrt{(2\pi \times 2 \times 10^3 \times 1 \times 10^{-3})^2 + 10^2} = 16.06$$

$$I_{o2} = \frac{V_{o2}}{Z_2} = \frac{18.71}{16.06} = 1.17\text{A (peak)}$$

$$V_{o3} = 12.47, Z_3 = 21.34, I_{o3} = 0.58\text{A (peak)}$$

$$V_{o4} = 15.14, Z_4 = 27.05, I_{o4} = 0.56\text{A (peak)}$$

$$V_{o5} = 0, Z_5 = 32.97, I_{o5} = 0\text{A}$$


Q: How to calculate rms value?

A: for h^{th} order harmonic,

$$\text{rms value} = \frac{\text{peak value}}{\sqrt{2}}$$

61


Example IV

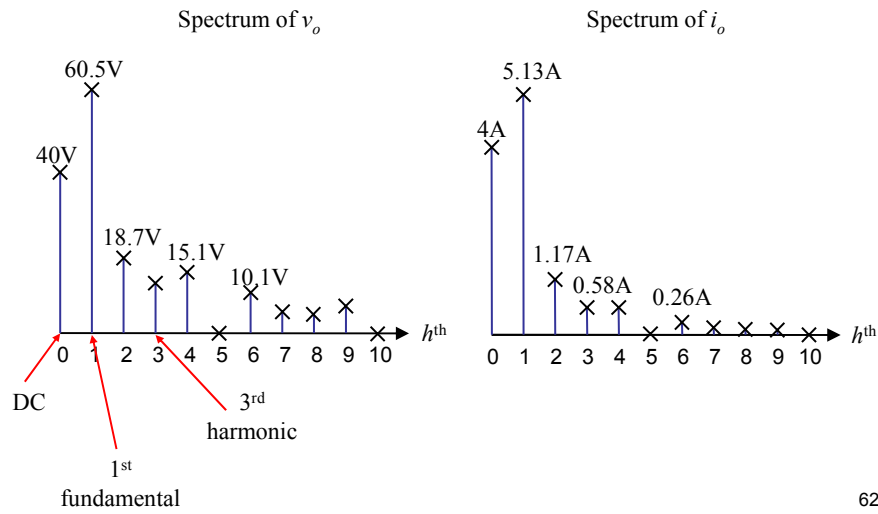


62

1.6 Two Quadrant Chopper

- Circuit diagram

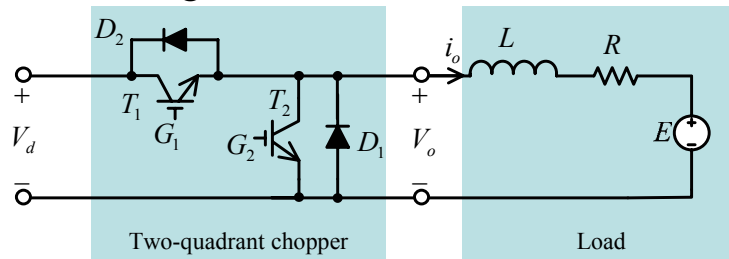


Bidirectional power flow

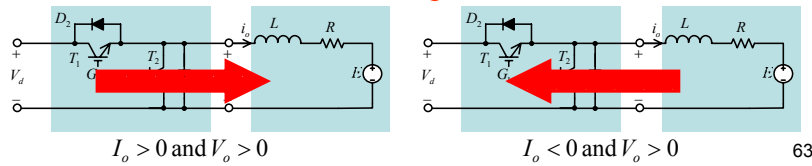

63

1.6 Two Quadrant Chopper

- Circuit diagram

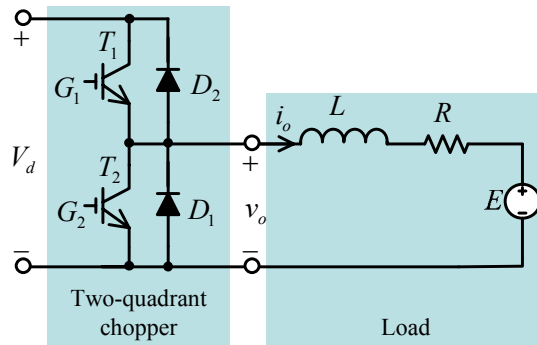


Applications:

- Battery control: charge or discharge the battery.
- DC motor drives: provide fast dynamic braking
- Any dc-dc applications need bidirectional power flow.

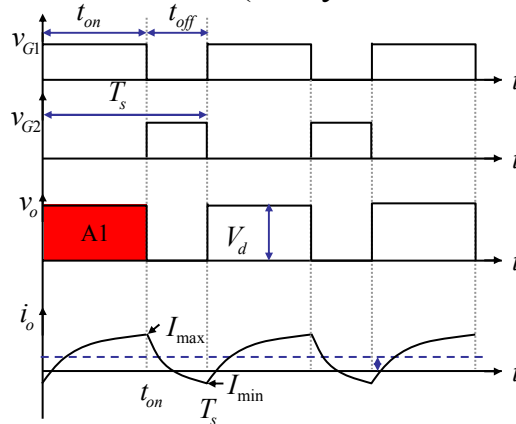1.6 Two Quadrant Chopper

- Waveforms (always continuous current mode)



when T_1/D_2 is on :

$$v_o = V_d = L \frac{di_o}{dt} + Ri_o + E \rightarrow$$

$$i_o(t) = \frac{V_d - E}{R} \left(1 - e^{-\frac{t}{\tau}} \right) + I_{min} e^{-\frac{t}{\tau}}$$

when T_2/D_1 is on :

$$v_o = 0 = L \frac{di_o}{dt} + Ri_o + E \rightarrow$$


$$i_o(t) = -\frac{E}{R} \left(1 - e^{-\frac{(t-t_{on})}{\tau}} \right) + I_{max} e^{-\frac{(t-t_{on})}{\tau}}$$

where $\tau = L/R$ is time constant of the load

$$V_{o,avg} = \frac{\text{Area A1}}{T_s} = \frac{V_d t_{on}}{T_s} = V_d \frac{t_{on}}{T_s} = DV_d$$

1.6 Two Quadrant Chopper

- Current waveforms

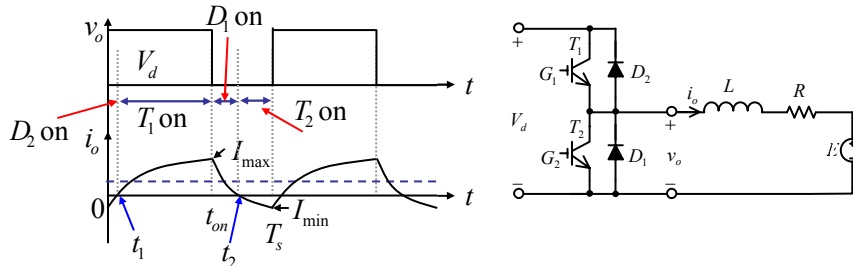


$0 \leq t < t_1$: The energy stored in L is releasing to V_d , D_2 is ON
 at t_1 : The energy stored in L is fully released
 $t_1 \leq t < t_{on}$: The energy from V_d is stored in L , $i_o \uparrow$, T_1 is ON
 $t_{on} \leq t < t_2$: The energy stored in L is releasing to R and E , D_1 is ON
 at t_2 : The energy stored in L is fully released
 $t_2 \leq t < T_s$: The energy from E is stored in L , $|i_o| \uparrow$, T_2 is ON

66

1.6 Two Quadrant Chopper

- Current paths

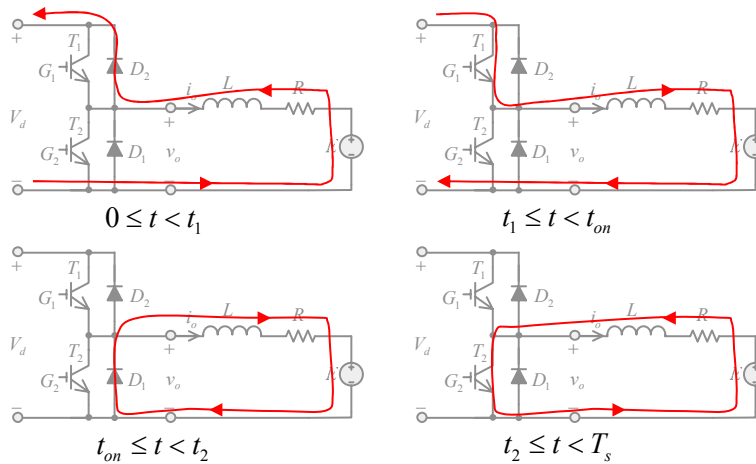


67

1.6 Two Quadrant Chopper

- I_{\max} and I_{\min}

From current waveform
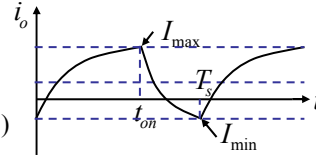
$$i_o(t) = \frac{V_d - E}{R} \left(1 - e^{-\frac{t}{\tau}} \right) + I_{\min} e^{-\frac{t}{\tau}}, 0 \leq t < t_{on} \quad (1)$$



$$i_o(t) = -\frac{E}{R} \left(1 - e^{-\frac{(t-t_{on})}{\tau}} \right) + I_{\max} e^{-\frac{(t-t_{on})}{\tau}}, t_{on} \leq t < T_s \quad (2)$$

From Eq.(1) At $t = t_{on}$, $i_o(t_{on}) = I_{\max} \rightarrow I_{\max} = \frac{V_d - E}{R} \left(1 - e^{-\frac{t_{on}}{\tau}} \right) + I_{\min} e^{-\frac{t_{on}}{\tau}} \quad (3)$

From Eq.(2) At $t = T_s$, $i_o(T_s) = I_{\min} \rightarrow I_{\min} = -\frac{E}{R} \left(1 - e^{-\frac{(T_s - t_{on})}{\tau}} \right) + I_{\max} e^{-\frac{(T_s - t_{on})}{\tau}} \quad (4)$

Solve Eq.(3) and Eq.(4)

$$I_{\max} = \frac{V_d}{R} \frac{1 - e^{-\frac{t_{on}}{\tau}}}{1 - e^{-\frac{T_s}{\tau}}} - \frac{E}{R} \quad \text{and} \quad I_{\min} = \frac{V_d}{R} \frac{e^{\frac{t_{on}}{\tau}} - 1}{e^{\frac{T_s}{\tau}} - 1} - \frac{E}{R}$$

Note: always continuous current mode!


68

1.7 Boost Converters

- Topology

Assumption:

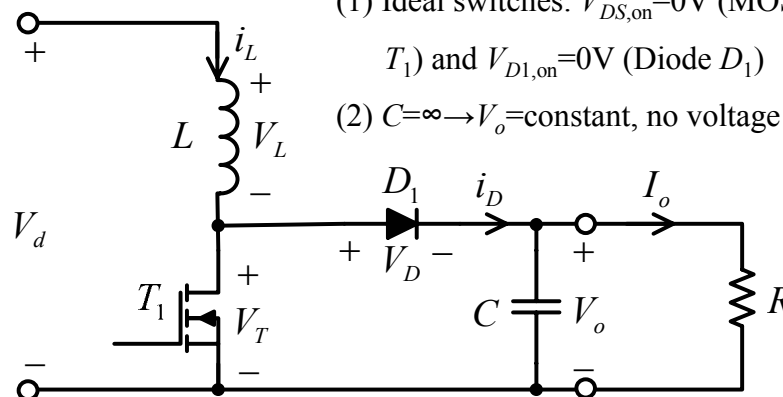
- (1) Ideal switches: $V_{DS,on} = 0V$ (MOSFET T_1) and $V_{D1,on} = 0V$ (Diode D_1)
- (2) $C = \infty \rightarrow V_o = \text{constant}$, no voltage ripple



69

1.7 Boost Converters


- Waveforms (continuous current mode)

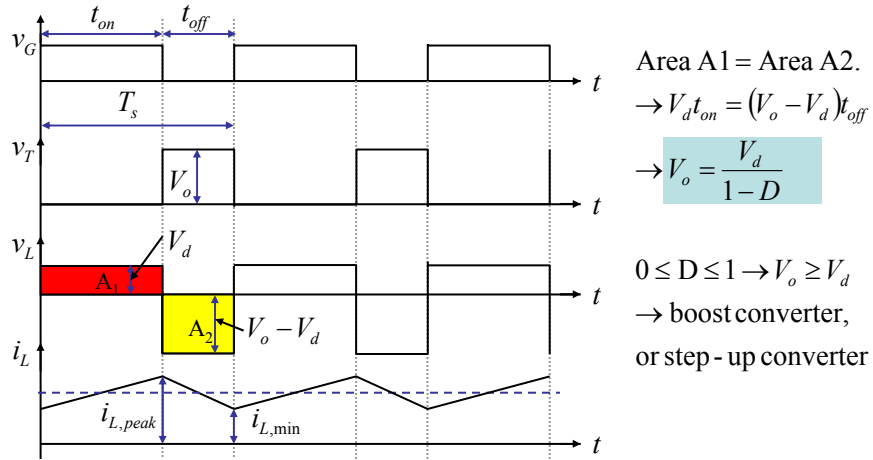

70

1.7 Boost Converters

- Output current

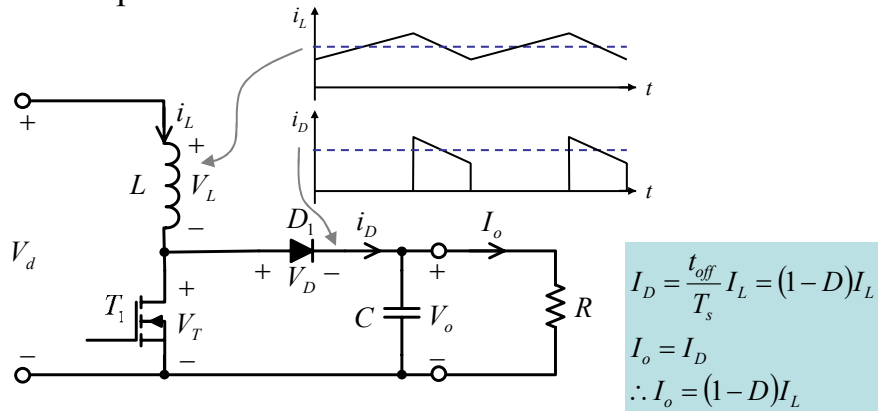



71

1.7 Boost Converters

- Boundary between continuous and discontinuous current mode

i_L continuous → continuous current mode

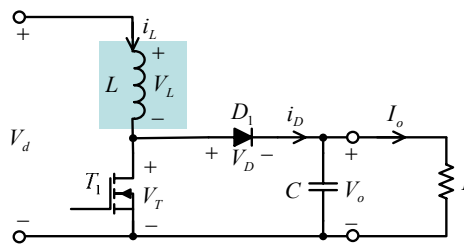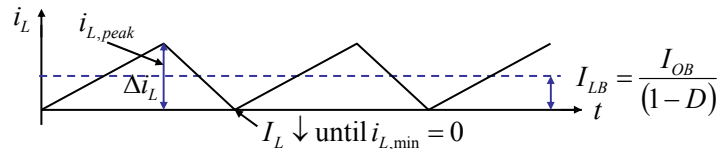i_L discontinuous → discontinuous current mode



$$v_L = L \frac{di_L}{dt} \rightarrow v_L = L \frac{\Delta i_L}{\Delta t} \rightarrow \Delta i_L = \frac{v_L}{L} \Delta t$$

During t_{on} , $v_L = V_d$

$$I_{LB} = \frac{1}{2} i_{L,peak} = \frac{1}{2} \frac{v_L}{L} \Delta t = \frac{1}{2} \frac{V_d}{L} t_{on} = \frac{1}{2L} V_d D T_s$$

$$\therefore I_{LB} = \frac{T_s V_o}{2L} D(1-D)$$

$$I_{OB} = \frac{T_s V_o}{2L} D(1-D)^2$$

72


1.7 Boost Converters

- Identify the operation mode of buck converter

$$I_{LB} = \frac{T_s V_o}{2L} D(1-D) \text{ or } I_{OB} = \frac{T_s V_o}{2L} D(1-D)^2$$

If $I_L > I_{LB}$ or $I_o > I_{OB} \rightarrow$ continuous current mode

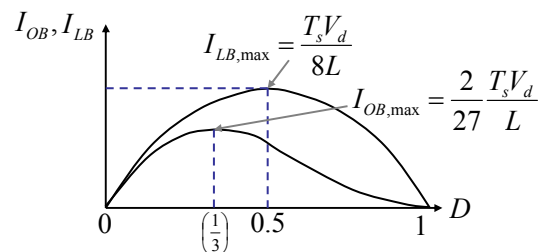
If $I_L < I_{LB}$ or $I_o < I_{OB} \rightarrow$ discontinuous current mode



73

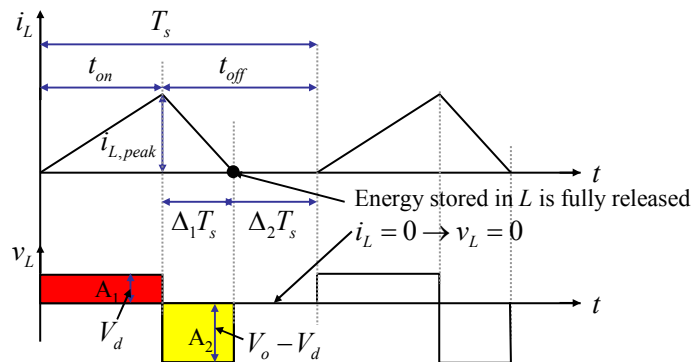1.7 Boost Converters

- Discontinuous current mode
 - Waveforms



74

1.7 Boost Converters

- Output voltage $V_o = ?$

Area $A_1 = \text{Area } A_2$

$$\rightarrow V_d D T_s = (V_o - V_d) \Delta_1 T_s \rightarrow V_o = \frac{D + \Delta_1}{\Delta_1} V_d \quad (1)$$

$$\Delta i_L = \frac{V_L}{L} \Delta t \rightarrow i_{L,peak} = \frac{V_o - V_d}{L} \Delta_1 T_s \rightarrow \Delta_1 = \frac{L i_{L,peak}}{(V_o - V_d) T_s} = \frac{I_o}{4 I_{LB,max} D} \quad (2)$$

$$(2) \rightarrow (1) V_o = \frac{D^2 + \frac{4}{27} \left(\frac{I_o}{I_{OB,max}} \right)}{\frac{4}{27} \left(\frac{I_o}{I_{OB,max}} \right)} V_d \quad \text{for discontinuous current mode}$$

if V_o is constant

$$D = \sqrt{\frac{4}{27} \left(\frac{V_o}{V_d} - 1 \right) \frac{I_o}{I_{OB,max}}}, \quad \text{where } I_{OB,max} = \frac{2}{27} \frac{T_s V_d}{L}$$

75


Summary

- Topologies: buck converter, one-quadrant chopper, two-quadrant chopper, boost converter, etc.
- Waveforms: current and voltage
- Operating mode and boundary (inductor current): continuous current mode or discontinuous current mode.
- DC component of voltage and current in two operating modes.
- Ripple current and ripple voltage
- Fourier analysis and high frequency equivalent circuits.

76

1.8 Isolated Switch Mode Power Supplies


- Flyback converter
 - Topology

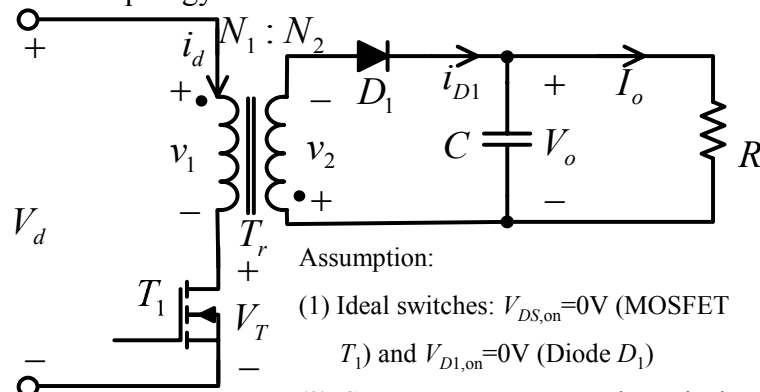

77

1.8 Isolated Switch Mode Power Supplies


– Waveforms (continuous current mode)

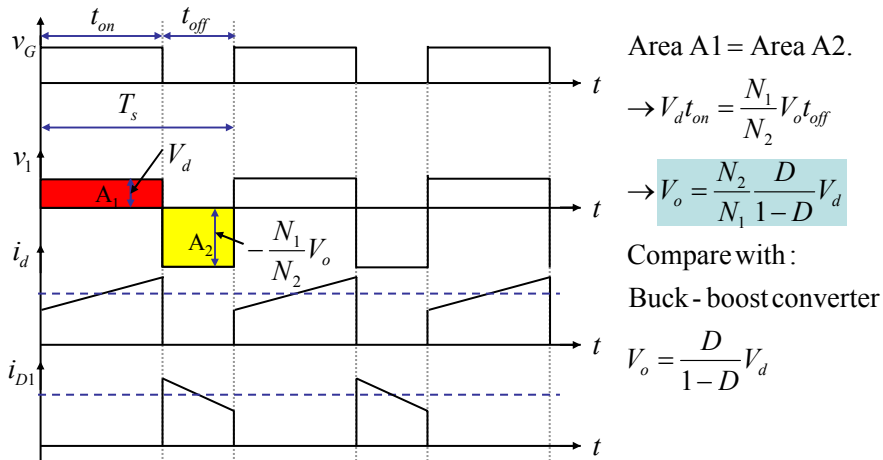

78

1.8 Isolated Switch Mode Power Supplies

– Analysis

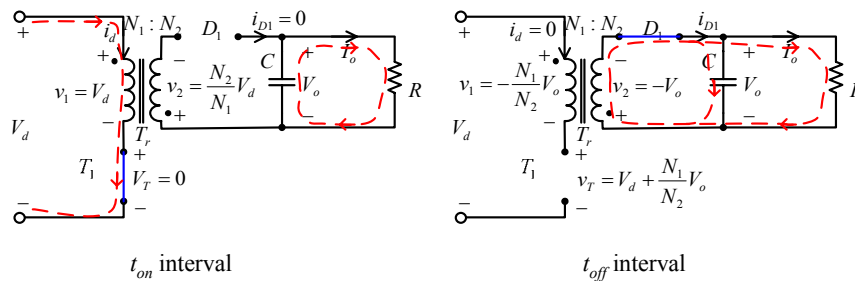

Note:

Energy is stored in the transformer
 $i_d \uparrow$, D_1 is off, the load is supplied by C

Note:


Energy stored in the transformer is released to C and load

$i_{d1} \downarrow$, D_1 is on.

79

1.8 Isolated Switch Mode Power Supplies


- Forward converter
 - Topology

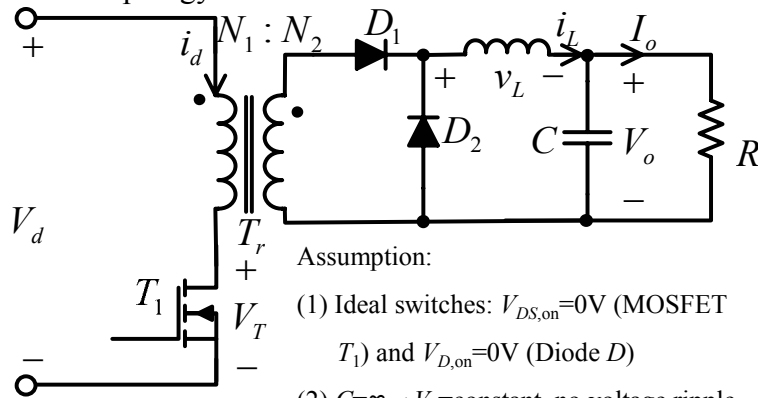

80

1.8 Isolated Switch Mode Power Supplies


- Waveforms (continuous current mode)

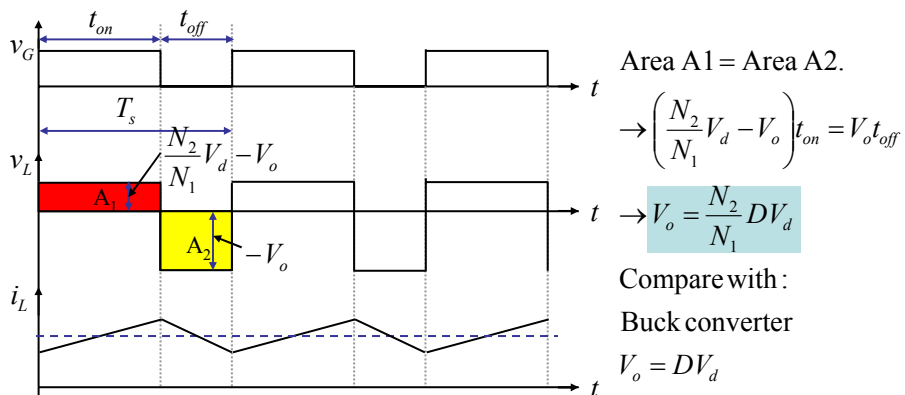

81

1.8 Isolated Switch Mode Power Supplies

- Practical design

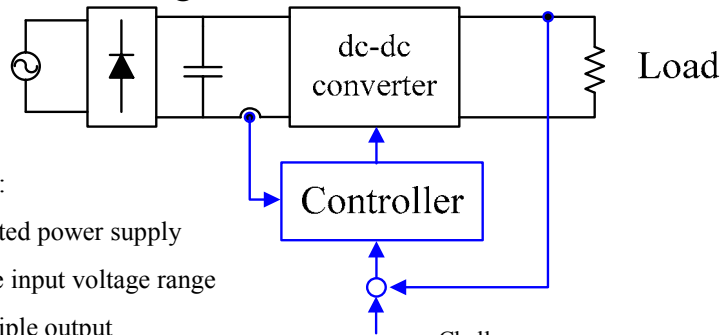

Features:

- (1) Isolated power supply
- (2) Wide input voltage range
- (3) Multiple output
- (4) Low utilization of the transformer

Challenges:

- (1) Improve efficiency
- (2) Compact size: $>50\text{W/in}^3$